

Lab Exercise No: 01

(1) (a) Study about computer system organization and architecture:

Discuss about functional components, types, generations and working aspects with respect to CISC and RISC architecture

(b) Study and implement the following using logisim simulator: (logic diagram / truth table / Boolean expression)

Basic and universal gates

De Morgan's theorem, associative law and distributive law

Adder and subtractor circuit

Boolean expression implementation as follows,

$$F1 = AB + CD$$

$$F2 = A'BC + C'B + ABC$$

$$F3 = AB' + BC' + CA'$$